

Name \_\_\_\_\_

## Series and Parallel Circuits: They're Electrifying!!

**Problem:** How do the behavior of series and parallel circuits compare?

**Research:**

**Hypothesis:**

### Materials

2 brads  
index card

3 light bulbs  
1 paperclip

2 batteries  
9 pieces insulated wire  
2 battery holders

### Procedure ~ Series Circuit

1. Using a battery, a light bulb, and wires, light up the bulb. Draw a diagram showing the flow of the current.

2. Construct a *series circuit* that contains a power source (1 battery), a resistor (light bulb), wires, and a switch. Draw a diagram showing the flow of the current, when the switch is open and when it is closed.

3. Repeat step 3 adding another resistor and another battery. Diagram your circuit showing the flow of current, when the switch is open and when it is closed.



3. In the circuit with three bulbs, remove one of the lights.

**Parallel Circuit Conclusion ~ Answer in COMPLETE sentences!!!**

- a. Explain what happens when the switch is opened and why. When the switch is closed?
  
- b. What happened to the brightness when you added resistors to the parallel circuit?
  
- c. In the parallel circuit, what happens when the first bulb is unconnected? Why?
  
- d. In the parallel circuit, what happens when the second bulb is unconnected (again with the first one reconnected)? Why?

**Conclusion ~ Answer in COMPLETE sentences!!!**

1. In which circuit did the two light bulbs appear brighter?
  
  
  
  
  
  
  
  
  
  
2. How do you know that you had a complete circuit?
  
  
  
  
  
  
  
  
  
  
3. What type of circuits do you think are in your house? Why?
  
  
  
  
  
  
  
  
  
  
4. Draw a diagram of a circuit that has both a series and a parallel circuit. If you have time, construct this circuit.